

Exercise Set 4 - Short Circuit Currents II

on

Power System Static Analysis

EEH - Power Systems Laboratory
ETH Zurich

26 October 2011



Eidgenössische Technische Hochschule Zürich
Swiss Federal Institute of Technology Zurich

1 Y- Δ connection

For the circuit below (in steady state) identify the short circuit current, in case of a three phase short circuit on point F. The generators nominal values are 200 MVA, 25 kV with $x''_{d1} = 0.2$ p.u.. Consider a constant prefault voltage over the circuit of $1\angle 0^\circ$ p.u.

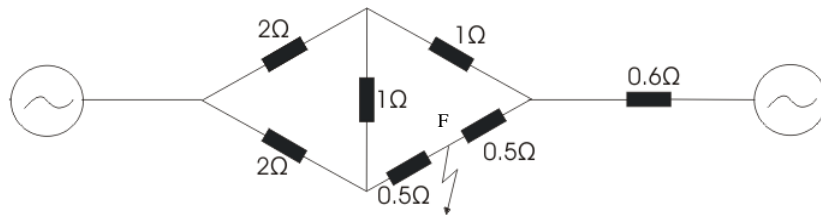


Figure 1: System for Exercise 1.

Hints:

- Use the Y- Δ transformation to simplify the network

2 Fault on a long-distance transmission line

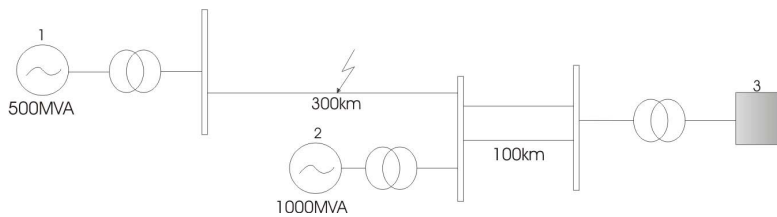


Figure 2: System for Exercise 2.

Two generators are connected to a infinite bus over 380 kV overhead-lines and 25/380 kV transformers as shown in Figure 2. Generator 1 has nominal values of 500 MVA, 25 kV with $x''_{d1} = 0.2$ p.u. and generator 2 of 1000 MVA, 25 kV with $x''_{d2} = 0.25$ p.u.. We select $S_B = 1000$ MVA, $V_B = 25$ kV on the low voltage side of the transformers and $V_B = 380$ kV on the high voltage side. The reactance of the transformers is 0.15 p.u. according to the selected base. The reactance of the lines is $0.25 \frac{\Omega}{\text{km}}$. The operating voltages in the terminals of generator 1 and 2 are $1\angle 3^\circ$ p.u. and $1\angle 3.5^\circ$ p.u. respectively.

The voltage of the infinite bus is $1\angle 0^\circ$ p.u.. Consider a three-phase short circuit at the middle point of the 300km line and calculate the sub-transient short circuit current.

3 Two-generator system

Consider the network of Figure 3, which is the same as we used for the Newton-Raphson iteration in the first exercise. The nominal values for the generators are 11 kV , 100 MVA , with subtransient reactance 0.1 p.u. . On the transmission lines all the shunt elements are capacitors with an admittance $y_C = 0.01\text{ p.u.}$, while all the series elements are inductors with an impedance of $z_L = 0.1\text{ p.u.}$. Consider a three phase fault on bus 3 and calculate the short circuit current.

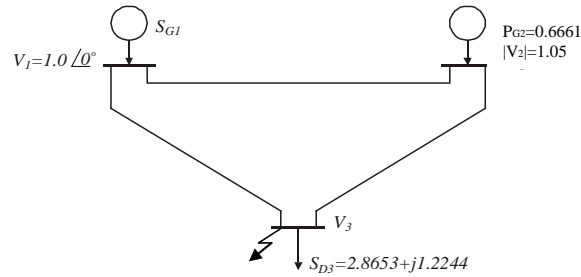


Figure 3: Simple two-generator system

Hints:

- Recall that you can disregard the loads for the short-circuit calculations (why?)
- Use the superposition technique
- You can use the results from exercise one. Please note that the admittance matrix changes due to the subtransient reactance, and the voltages at node 1 and 2 will be influenced by the short circuit